

# Laplace Transforms

Mohammad Hadi

*mohammad.hadi@sharif.edu*

*@MohammadHadiDastgerdi*

Fall 2021

# Overview

1 Laplace Transform

2 Laplace Analysis

# Laplace Transform

## Definition (Laplace Transform)

The unidirectional Laplace transform of  $f(t)$  is defined as

$$F(s) = \mathcal{L}[f(t)] = \int_{0^-}^{\infty} f(t)e^{-st} dt, \quad s \in \text{ROC}$$

, where ROC is the region of convergence representing complex values of  $s$  for which the Laplace integral converges.  $f(t)$  can be calculated from its Laplace transform as

$$f(t) = \mathcal{L}^{-1}[F(s)] = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s)e^{st} ds, \quad \sigma \in \text{ROC}$$

# Laplace Transform

## Example (Laplace transform of $u(t)$ )

$$\mathcal{L}[u(t)] = \frac{1}{s}, \quad \Re\{s\} > 0.$$

$$\int_{0^-}^{\infty} f(t)e^{-st} dt = \int_0^{\infty} e^{-st} dt = \left. \frac{-e^{-st}}{s} \right|_0^{\infty} = \left. \frac{-e^{-(\sigma+j\omega)t}}{s} \right|_0^{\infty} = \frac{1}{s}, \quad \Re\{s\} > 0$$

## Example (Laplace transform of $e^{-at}u(t)$ )

$$\mathcal{L}[e^{-at}u(t)] = \frac{1}{s+a}, \quad \Re\{s\} > \Re\{-a\}.$$

$$\int_{0^-}^{\infty} f(t)e^{-st} dt = \int_0^{\infty} e^{-at}e^{-st} dt = \left. \frac{-e^{-(s+a)t}}{s+a} \right|_0^{\infty} = \left. \frac{-e^{-(s+a)t}}{s+a} \right|_0^{\infty} = \frac{1}{s+a}, \quad \Re\{s\} > \Re\{-a\}$$

# Laplace Transform Properties

Property	Time Domain	Laplace Domain
Linearity	$\alpha f_1(t) + \beta f_2(t)$	$\alpha F_1(s) + \beta F_2(s)$
Time Shift	$f(t - t_0)u(t - t_0)$	$e^{-st_0} F(s)$
Frequency Shift	$e^{s_0 t} f(t)$	$F(s - s_0)$
Scaling	$f(\alpha t), \alpha > 0$	$\frac{1}{\alpha} F(\frac{s}{\alpha})$
Conjugation	$f^*(t)$	$\bar{F}^*(s^*)$
Time Differentiation	$f'(t)$	$sF(s) - f(0^-)$
Time Differentiation	$f''(t)$	$s^2 F(s) - sf(0^-) - f'(0^-)$
Frequency Differentiation	$tf(t)$	$-X'(s)$
Time Integration	$\int_0^\infty f(\alpha) d\alpha$	$F(s)/s$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$
Periodicity	$f(t + T) = f(t)$	$\int_0^{T-} f(t)e^{-st} dt / (1 - e^{-sT})$
Initial Value	$f(0^+) = \lim_{s \rightarrow \infty} sF(s)$	
Final Value	$f(+\infty) = \lim_{s \rightarrow 0} sF(s)$	

**Table: Properties of Laplace transform.** For convolution property,  $f_1(t) = 0, t < 0$  and  $f_2(t) = 0, t < 0$ . For initial value and final value properties,  $f(t) = 0, t < 0$  and has no singular function at  $t = 0$ .

# Laplace Transform Pairs

Time Domain	Laplace Domain
$\delta(t)$	1
$\delta'(t)$	$s$
$\delta^{(n)}(t)$	$s^n$
$u(t)$	$\frac{1}{s}$
$tu(t)$	$\frac{1}{s^2}$
$t^n u(t)$	$\frac{n!}{s^{n+1}}$
$e^{-at}u(t)$	$\frac{1}{s+a}$
$t^n e^{-at}u(t)$	$\frac{n!}{(s+a)^{n+1}}$
$\cos(\beta t)u(t)$	$\frac{s}{s^2+\beta^2}$
$\sin(\beta t)u(t)$	$\frac{\beta}{s^2+\beta^2}$

Table: Useful Laplace pairs.

Time Domain	Laplace Domain
$\cosh(\beta t)u(t)$	$\frac{s}{s^2-\beta^2}$
$\sinh(\beta t)u(t)$	$\frac{\beta}{s^2-\beta^2}$
$e^{-at} \cos(\beta t)u(t)$	$\frac{s+a}{(s+a)^2+\beta^2}$
$e^{-at} \sin(\beta t)u(t)$	$\frac{\beta}{(s+a)^2+\beta^2}$
$t \cos(\beta t)u(t)$	$\frac{s^2-\beta^2}{(s^2+\beta^2)^2}$
$t \sin(\beta t)u(t)$	$\frac{2\beta s}{(s^2+\beta^2)^2}$
$\cos(\beta t + \phi)u(t)$	$\frac{s \cos(\phi) - \beta \sin(\phi)}{s^2+\beta^2}$
$2 K e^{-at} \cos(\beta t + \angle K)u(t)$	$\frac{K}{s+a-j\beta} + \frac{K^*}{s+a+j\beta}$
$2 K te^{-at} \cos(\beta t + \angle K)u(t)$	$\frac{K}{(s+a-j\beta)^2} + \frac{K^*}{(s+a+j\beta)^2}$

Table: Useful Laplace pairs.

## Example (Laplace Transform)

$$\mathcal{L}[t \cos(\beta t)u(t)] = \frac{s^2 - \beta^2}{s^2 + \beta^2}$$

$$e^{-at}u(t) \rightarrow \frac{1}{s+a}$$

$$e^{-j\beta t}u(t) \rightarrow \frac{1}{s+j\beta}$$

$$\cos(\beta t)u(t) = 0.5(e^{j\beta t} + e^{-j\beta t})u(t) \rightarrow 0.5\left(\frac{1}{s-j\beta} + \frac{1}{s+j\beta}\right) = \frac{s}{s^2 + \beta^2}$$

$$t \cos(\beta t)u(t) \rightarrow -\frac{d}{ds} \left[ \frac{s}{s^2 + \beta^2} \right] = \frac{s^2 - \beta^2}{(s^2 + \beta^2)^2}$$



# Fractional Functions

- Real-coefficient rational function:

$$F(s) = \frac{P(s)}{Q(s)} = \frac{\sum_{l=0}^m b_l s^l}{\sum_{k=0}^n a_k s^k}, \quad a_i, b_i \in \mathbb{R}, s \in \mathbb{C}$$

- Transfer function zeros:  $\{z_i \in \mathcal{C} | P(z_i) = 0\}$

- Transfer function poles:  $\{p_i \in \mathcal{C} | Q(p_i) = 0\}$

- Zero-pole decomposition:  $F(s) = \frac{P(s)}{Q(s)} = K \frac{\prod_{l=1}^m (s - z_l)}{\prod_{k=1}^n (s - p_k)}$

- Proper rational function:  $F(s) = \frac{P(s)}{Q(s)} = \frac{\sum_{l=0}^m b_l s^l}{\sum_{k=0}^n a_k s^k}, \quad a_i, b_i \in \mathbb{R}, s \in \mathbb{C}, m < n$

- Proper rational-polynomial function decomposition:

$$F(s) = \frac{P(s)}{Q(s)} = \hat{P}(s) + \frac{R(s)}{Q(s)}$$

# Partial-fraction Expansion

## Definition (Partial-fraction Expansion)

A proper fractional function is decomposed as

$$F(s) = \frac{R(s)}{Q(s)} = \frac{R(s)}{\prod_{k=1}^r (s - p_k)^{n_k}} = \sum_{i=1}^r \sum_{j=1}^{n_i} \frac{K_{i,j}}{(s - p_i)^j}$$

, where

$$K_{i,n_i-l} = \frac{1}{l!} \frac{d^l}{ds^l} [(s - p_i)^{n_i} F(s)] \Big|_{s=p_i}, \quad l = 0, 1, \dots, n_i - 1$$

# Inverse Laplace Transform

## Example (Proper rational Laplace function with two simple poles)

$$\mathcal{L}^{-1}\left[\frac{s+3}{(s+1)(s+2)}\right] = (2e^{-t} - e^{-2t})u(t)$$

$$F(s) = \frac{s+3}{(s+1)(s+2)} = \frac{K_{11}}{s+1} + \frac{K_{21}}{s+2}$$

$$K_{11} = (s+1)F(s)|_{s=-1} = \frac{s+3}{s+2}|_{s=-1} = 2, \quad K_{21} = (s+2)F(s)|_{s=-2} = \frac{s+3}{s+1}|_{s=-2} = -1$$

$$F(s) = \frac{s+3}{(s+1)(s+2)} = \frac{2}{s+1} + \frac{-1}{s+2}$$

$$F(s) = \frac{s+3}{(s+1)(s+2)} = \frac{K_{11}}{s+1} + \frac{K_{21}}{s+2} = \frac{(K_{11} + K_{21})s + (2K_{11} + K_{21})}{(s+1)(s+2)}$$

$$\begin{cases} K_{11} + K_{21} = 1 \\ 2K_{11} + K_{21} = 3 \end{cases} \Rightarrow \begin{cases} K_{11} = 2 \\ K_{21} = -1 \end{cases}$$

$$F(s) = \frac{s+3}{(s+1)(s+2)} = \frac{2}{s+1} + \frac{-1}{s+2}$$

$$f(t) = (2e^{-t} - e^{-2t})u(t)$$

# Inverse Laplace Transform

## Example (Improper rational Laplace function with two simple poles)

$$\mathcal{L}^{-1}\left[\frac{s^2+1}{s(s+1)}\right] = \delta(t) + (1 - 2e^{-t})u(t)$$

$$F(s) = \frac{s^2+1}{s(s+1)} = 1 + \frac{-s+1}{s(s+1)} = 1 + \frac{K_{11}}{s} + \frac{K_{21}}{s+1}$$

$$K_{11} = \frac{-s+1}{s+1} \Big|_{s=0} = 1, \quad K_{21} = \frac{-s+1}{s} \Big|_{s=-1} = -2$$

$$F(s) = \frac{s^2+1}{s(s+1)} = 1 + \frac{-s+1}{s(s+1)} = 1 + \frac{1}{s} + \frac{-2}{s+1}$$

$$f(t) = \delta(t) + (1 - 2e^{-t})u(t)$$

# Inverse Laplace Transform

Example (Proper rational Laplace function with simple, repeated, and complex poles)

$$\mathcal{L}^{-1}\left[\frac{4s^4+19s^3+36s^2+34s+16}{(s+2)(s+1)^2(s^2+2s+2)}\right] = [2e^{-2t} + 2e^{-t} + 3te^{-t} + 2\sqrt{2}e^{-t}\cos(t + \underline{45^\circ})]u(t)$$

$$F(s) = \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+2)(s+1)^2(s^2+2s+2)} = \frac{K_{11}}{s+2} + \frac{K_{21}}{s+1} + \frac{K_{22}}{(s+1)^2} + \frac{K_{31}}{s+1-j} + \frac{K_{41}}{s+1+j}$$

$$K_{11} = \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+1)^2(s^2+2s+2)} \Big|_{s=-2} = 2$$

$$K_{21} = \frac{d}{ds} \left[ \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+2)(s^2+2s+2)} \right] \Big|_{s=-1} = 2$$

$$K_{22} = \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+2)(s^2+2s+2)} \Big|_{s=-1} = 3$$

$$K_{31} = \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+2)(s+1)^2(s+1+j)} \Big|_{s=-1+j} = 1+j$$

$$K_{41} = \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+2)(s+1)^2(s+1-j)} \Big|_{s=-1-j} = 1-j$$

$$F(s) = \frac{4s^4 + 19s^3 + 36s^2 + 34s + 16}{(s+2)(s+1)^2(s^2+2s+2)} = \frac{2}{s+2} + \frac{2}{s+1} + \frac{3}{(s+1)^2} + \frac{1+j}{s+1-j} + \frac{1-j}{s+1+j}$$

$$f(t) = [2e^{-2t} + 2e^{-t} + 3te^{-t} + 2\sqrt{2}e^{-t}\cos(t + \underline{45^\circ})]u(t)$$

# Inverse Laplace Transform

## Example (Proper rational Laplace function with repeated complex poles)

$$\mathcal{L}^{-1}\left[\frac{768}{(s^2+6s+25)^2}\right] = \left[6e^{-3t} \cos(4t + \underline{90^\circ}) - 24te^{-3t} \cos(4t)\right] u(t)$$

$$F(s) = \frac{768}{(s^2 + 6s + 25)^2} = \frac{K_{11}}{s + 3 - 4j} + \frac{K_{12}}{(s + 3 - 4j)^2} + \frac{K_{21}}{s + 3 + 4j} + \frac{K_{22}}{(s + 3 + 4j)^2}$$

$$K_{11} = \frac{d}{ds} \left[ \frac{768}{(s + 3 + 4j)^2} \right] \Big|_{s=-3+4j} = -3j$$

$$K_{12} = \frac{768}{(s + 3 + 4j)^2} \Big|_{s=-3+4j} = -12$$

$$K_{21} = \frac{d}{ds} \left[ \frac{768}{(s + 3 - 4j)^2} \right] \Big|_{s=-3-4j} = +3j$$

$$K_{22} = \frac{768}{(s + 3 - 4j)^2} \Big|_{s=-3-4j} = -12$$

$$F(s) = \frac{768}{(s^2 + 6s + 25)^2} = \frac{-3j}{s + 3 - 4j} + \frac{-12}{(s + 3 - 4j)^2} + \frac{3j}{s + 3 + 4j} + \frac{-12}{(s + 3 + 4j)^2}$$

$$f(t) = \left[6e^{-3t} \cos(4t + \underline{90^\circ}) - 24te^{-3t} \cos(4t)\right] u(t)$$

# Laplace Analysis

# Circuit Analysis

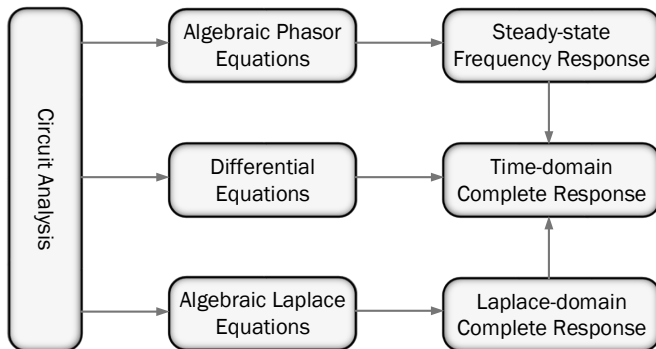


Figure: Different methods of **circuit analysis**.



# Laplace Analysis

## Example (First-order RC circuit)

The complete response to the impulse and step inputs for a first-order circuit can be found using Laplace transform.

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = i_s(t), \quad v_C(0^-) = V_0$$


$$\frac{dv_C(t)}{dt} + \frac{v_C(t)}{RC} = \frac{\delta(t)}{C} \Rightarrow (sV_C(s) - V_0) + \frac{V_C(s)}{RC} = \frac{1}{C}$$

$$V_C(s) = \frac{\frac{1}{C} + V_0}{s + \frac{1}{RC}} \Rightarrow v_C(t) = \left[ \frac{1}{C} + V_0 \right] e^{-\frac{t}{RC}} u(t), \quad t \geq 0$$

$$\frac{dv_C(t)}{dt} + \frac{v_C(t)}{RC} = \frac{u(t)}{C} \Rightarrow (sV_C(s) - V_0) + \frac{V_C(s)}{RC} = \frac{1}{Cs}$$

$$V_C(s) = \frac{V_0}{s + \frac{1}{RC}} + \frac{R}{s} - \frac{R}{s + \frac{1}{RC}}$$
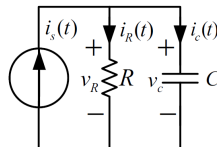
$$v_C(t) = V_0 e^{-\frac{t}{RC}} u(t) + R(1 - e^{-\frac{t}{RC}}) u(t), \quad t \geq 0$$



# Complete Response

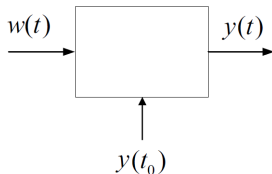


Figure: Laplace transform for **constant-coefficient linear differential equations**. Laplace analysis confirms that for linear systems, the complete response is the sum of zero-input and zero-state responses.

$$\sum_{k=0}^n a_k y^{(k)}(t) = \sum_{l=0}^m b_l w^{(l)}(t), \quad y(0^-), y'(0^-), \dots, y^{(n-1)}(0^-)$$

$$\sum_{k=0}^n [a_k s^k Y(s) - \sum_{k'=1}^k s^{k-k'} y^{(k'-1)}(0^-)] = \sum_{l=0}^m b_l s^l W(s)$$

$$Y(s) \sum_{k=0}^n a_k s^k - F_0(s) = W(s) \sum_{l=0}^m b_l s^l$$

$$Y(s) = \frac{\sum_{l=0}^m b_l s^l}{\sum_{k=0}^n a_k s^k} W(s) + \frac{F_0(s)}{\sum_{k=0}^n a_k s^k}$$

$$Y(s) = H(s)W(s) + \frac{F_0(s)}{\sum_{k=0}^n a_k s^k}$$

# Zero-state Response



Figure: **Transfer function** for zero-state response of LTI systems.

- **Laplace-domain zero-state response:**  $Y(s) = H(s)W(s)$
- **Transfer function:**  $H(s) = \frac{\sum_{l=0}^m b_l s^l}{\sum_{k=0}^n a_k s^k}$
- **Transfer function zeros:**  $\{s_i \in \mathcal{C} | H(s_i) = 0\}$
- **Transfer function poles:**  $\{s_i \in \mathcal{C} | H(s_i) = \infty\}$
- **Time-domain zero-state response:**  $y(t) = h(t) * w(t)$ ,  $h(t) = \mathcal{L}^{-1}[H(s)]$
- **Frequency response:**  $H(j\omega) = H(s)|_{s=j\omega}$
- **Multi-input zero-state response:**  $Y(s) = \sum_i H_i(s)W_i(s)$ ,  $H_i(s) = \frac{Y(s)}{W_i(s)}|_{W_k(s)=0, k \neq i}$

# Impedance and Admittance

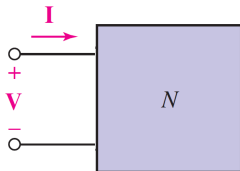


Figure: Impedance  $Z(s) = \frac{V(s)}{I(s)}$  and admittance  $Y(s) = \frac{I(s)}{V(s)} = \frac{1}{Z(s)}$  for a **one-port** network containing no independent sources and initial conditions.

Element	Impedance $Z(s) = \frac{V(s)}{I(s)}$	Admittance $Y(s) = \frac{I(s)}{V(s)}$
Resistor	$R$	$G$
Capacitor	$\frac{1}{Cs}$	$Cs$
Inductor	$jLs$	$\frac{1}{Ls}$

Table: Impedance and admittance for basic LTI one-port circuit elements. **Series** and **parallel** combinations as well as **delta-why** conversion can be used for impedance and admittance.

# Impedance and Admittance

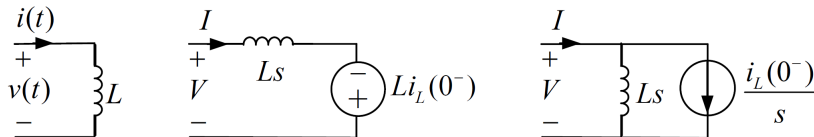


Figure: Series and parallel model of LTI inductor with initial condition in Laplace-domain.

- Time-domain element equation:  $v(t) = Li'(t), \quad i_L(0^-)$
- Series Laplace-domain element equation:  $V(s) = LsI(s) - Li_L(0^-)$
- Parallel Laplace-domain element equation:  $I(s) = \frac{V(s)}{Ls} + \frac{i_L(0^-)}{s}$

# Impedance and Admittance

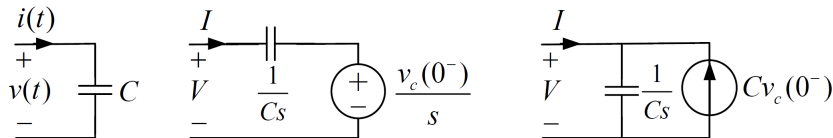



Figure: Series and parallel model of LTI capacitor with initial condition in Laplace-domain.

- Time-domain element equation:  $i(t) = Cv'(t), \quad v_c(0^-)$
- Parallel Laplace-domain element equation:  $I(s) = CsV(s) - Cv_c(0^-)$
- Series Laplace-domain element equation:  $V(s) = \frac{I(s)}{Cs} + \frac{v_c(0^-)}{s}$

# Impedance and Admittance
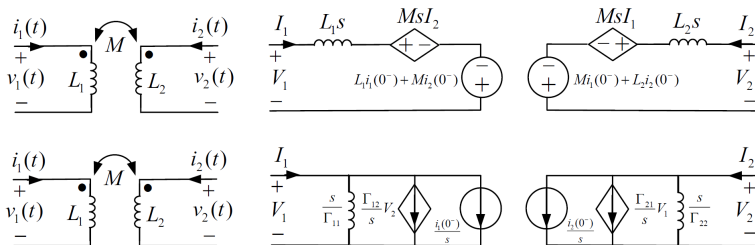
## Example (Laplace model of coupled inductors)

Coupled inductors can be modeled in Laplace domain using dependent sources.



$$\begin{cases} v_1(t) = L_1 i_1'(t) + M i_2'(t) \\ v_2(t) = M i_1'(t) + L_2 i_2'(t) \end{cases}, \quad i_1(0^-), i_2(0^-)$$

$$\begin{cases} V_1(s) = L_1 s I_1(s) + M s I_2(s) - (L_1 i_1(0^-) + M i_2(0^-)) \\ V_2(s) = M s I_1(s) + L_2 s I_2(s) - (M i_1(0^-) + L_2 i_2(0^-)) \end{cases}$$

$$\begin{cases} I_1(s) = \frac{\Gamma_{11}}{s} V_1(s) + \frac{\Gamma_{12}}{s} V_2(s) + \frac{i_1(0^-)}{s} \\ I_2(s) = \frac{\Gamma_{21}}{s} V_1(s) + \frac{\Gamma_{22}}{s} V_2(s) + \frac{i_2(0^-)}{s} \end{cases}$$

# Laplace Analysis

## Example (First-order RC circuit)

The complete response to the impulse and step inputs for a first-order circuit can be found using Laplace transform.

$$-I_s(s) + \frac{V_C(s)}{R} + \frac{V_C(s)}{1/Cs} - CV_0 = 0 \Rightarrow V_C(s) = \frac{\frac{I_s(s)}{C} + V_0}{s + \frac{1}{RC}}$$


$$I_s(s) = 1 \Rightarrow V_C(s) = \frac{\frac{1}{C} + V_0}{s + \frac{1}{RC}}$$

$$v_C(t) = \left[\frac{1}{C} + V_0\right]e^{-\frac{t}{RC}}u(t), t \geq 0$$

$$I_s(s) = \frac{1}{s} \Rightarrow V_C(s) = \frac{\frac{1}{Cs} + V_0}{s + \frac{1}{RC}}$$

$$V_C(s) = \frac{V_0}{s + \frac{1}{RC}} + \frac{R}{s} - \frac{R}{s + \frac{1}{RC}}$$
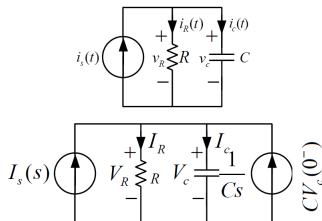
$$v_C(t) = V_0 e^{-\frac{t}{RC}}u(t) + R(1 - e^{-\frac{t}{RC}})u(t), t \geq 0$$





# Laplace Analysis


## Example (Coupled circuit)

A coupled circuit can be analyzed using Laplace transform.

$$i_1(0^-) = 50 \frac{6 \parallel 5}{6 \parallel 5 + 20} = 6$$

$$i_2(0^-) = 50 \frac{6 \parallel 20}{6 \parallel 20 + 5} = 24$$

$$v(0^-) = 5i_2(0^-) = 120$$

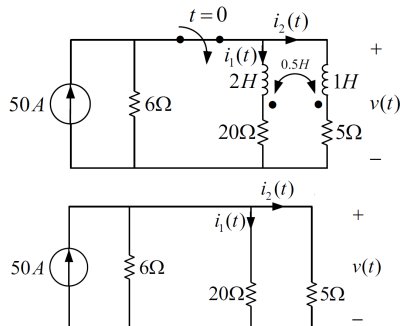

# Laplace Analysis

## Example (Coupled circuit)

A coupled circuit can be analyzed using Laplace transform.


$$\begin{cases} 20i_2 + 24 - 0.5si_2 + 2si_2 + si_2 + 0.5si_1 - 27 + 5i_2 = 0 \\ i_1 = -i_2 \end{cases}$$

$$i_2(s) = \frac{1.5}{s + 12.5} \Rightarrow i_2(t) = -i_1(t) = 1.5e^{-12.5t}u(t)$$

$$V(s)2si_1 + 0.5si_2 - 24 + 20i_1 = (1.5s + 20)i_1 - 24$$

$$V(s) = \frac{-105}{4} - \frac{15}{8} \frac{1}{s + 12.5}$$
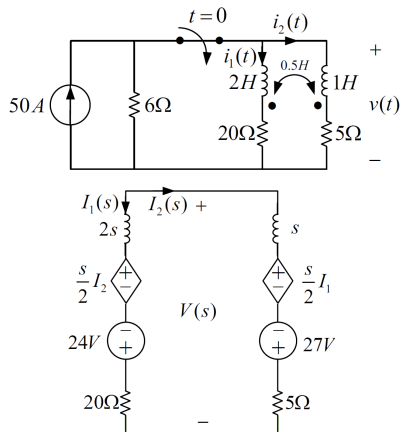
$$v(t) = \frac{-105}{4} \delta(t) - \frac{15}{8} e^{-12.5t} u(t)$$



# The End